

---

## ELEX 7660 Team #1 Report

Neil Dehoog  
Joshua Lang  
Set 6T

# Automated Fishing Hook

9<sup>th</sup> April 2018

Introduction and Objectives	2
Achievement	2
Operation	2
Resources	7
Conclusion	7
Appendix A: Code	8
SV Module: Fish.sv Top Level	8
SV Module: Control.sv	10
SV Module: Colseq.sv	12
SV Module: Decode7.sv	12
SV Module: kpdecode.sv	13
SV Module: mode.sv	14
SV Module: motor.sv	14
SV Module: motor_decode.sv	16
SV Module: optics.sv	16
SV Module: pulse.sv	16

---

Figure 1: Block diagram of the overall system	2
Figure 2: Block diagram of Mode.sv	3
Figure 3: Block diagram of Motor.sv	3
Figure 4: Block diagram Motor_decode.sv	4
Figure 5: Block diagram for the pulse.sv	5
Figure 6: Block diagram of colseq.sv	5
Figure 7: Block diagram for optics.sv	5
Figure 8: Block diagram for decode7.sv	6

---

## Introduction and Objectives

This project was initiated as a means of increasing the efficiency of downrigger fishing devices. The efficiency of these devices is directly related to their ability to maintain a set distance off of the bottom of the ocean floor. We made a proof of concept model that could achieve a fixed distance above a floating reference point. To do this we utilized the following hardware:

- Close range IR sensor to prevent over reeling in
- Ultrasonic distance sensor to gauge ground distance
- Stepper motor to accurately control line length
- SPST switch to toggle between manual mode and autonomous
- 4x4 keypad to control line level manually
- 7-segment display to show which key is being utilized
- Cyclone IV FPGA board as a control system

For the construction of the control system we programmed the FPGA board using Quartus v17.1 and monitored key sensor outputs using the Quartus signaltap addon.

## Achievement

We have achieved all of our set objectives for the automated fishing hook:

- Using the code we written for the keypad to control the motor in manual operations of the fishing hook.
- Used an ultrasonic distance sensor to measure distance to the artificial ground.
- In order to reel in the fishing line we used a stepper motor for the controllability.
- An optic sensor was used to stop the reel going to far.
- An basic SPST switch was used to control operation modes

## Operation

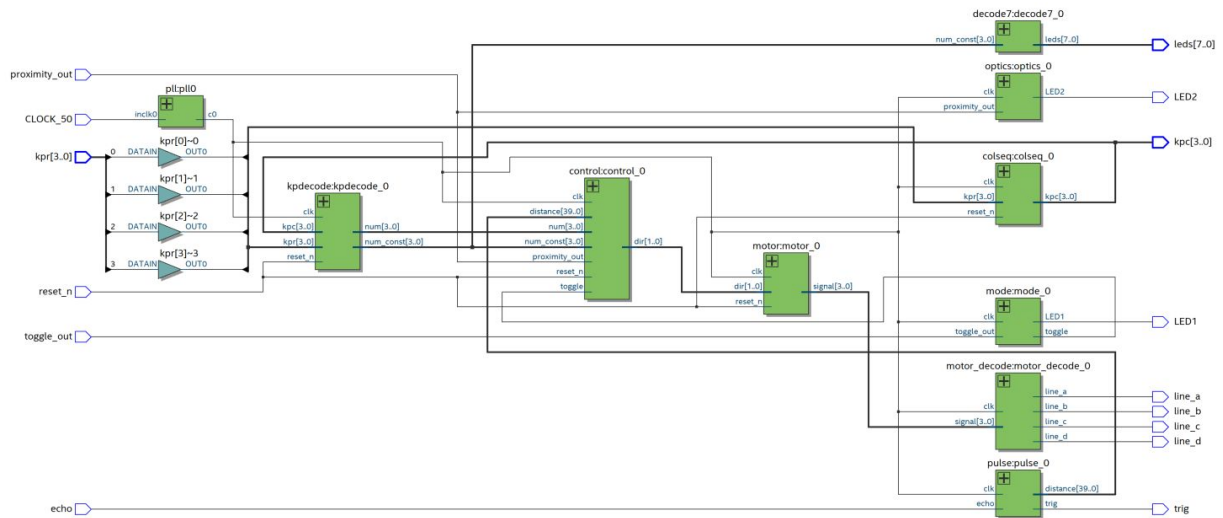


Figure 1: Block diagram of the overall system

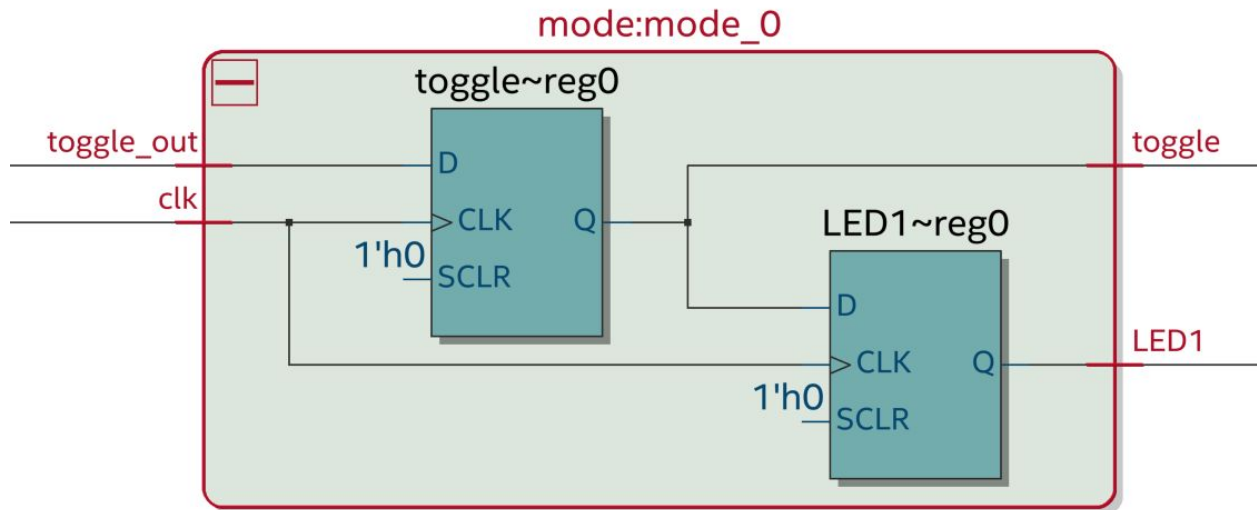


Figure 2: Block diagram of Mode.sv



 


Figure 4: Block diagram Motor\_decode.sv

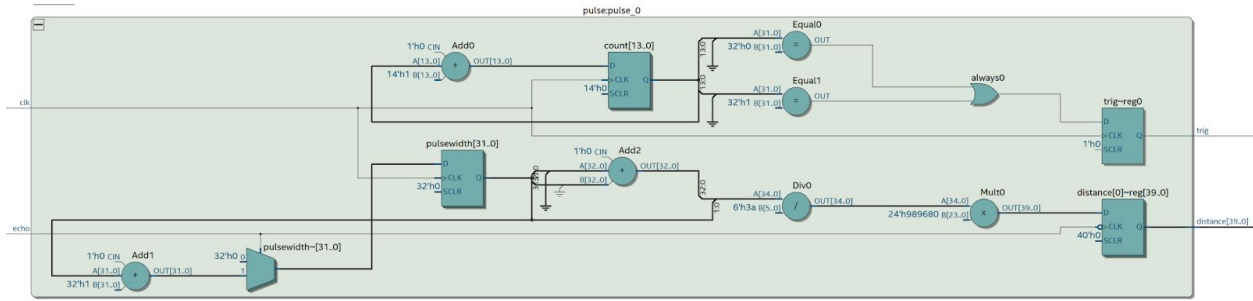


Figure 5: Block diagram for the pulsepulse\_0

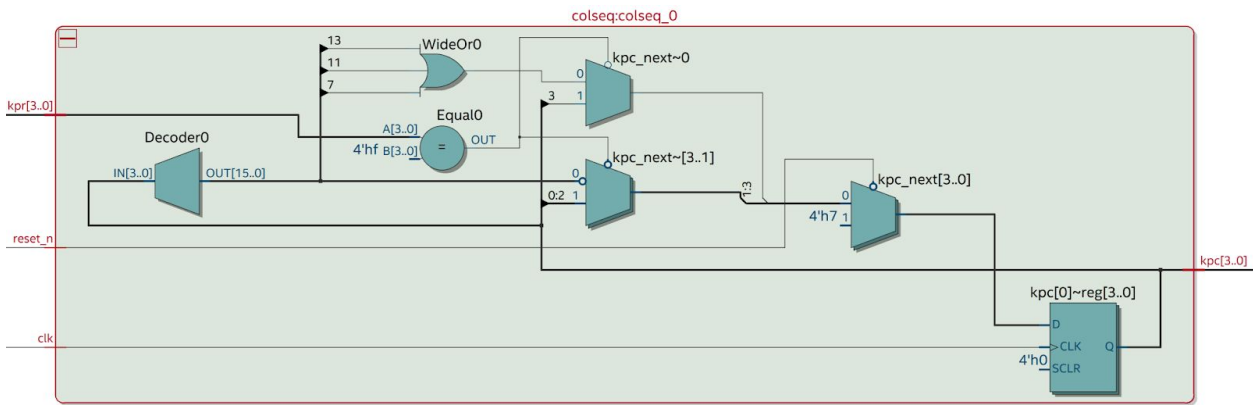


Figure 6: Block diagram of colseq\_0

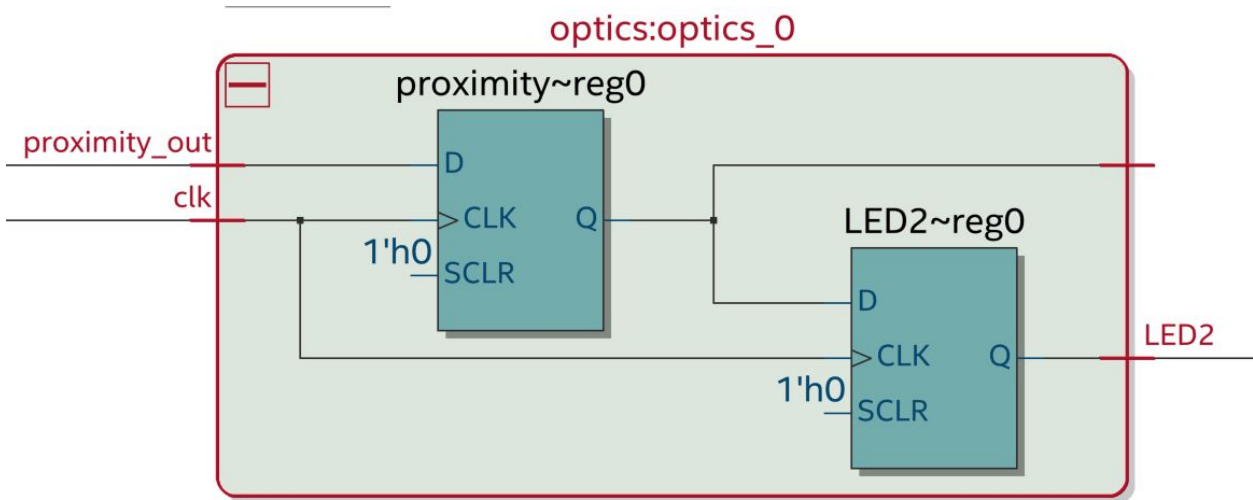


Figure 7: Block diagram for optics\_0

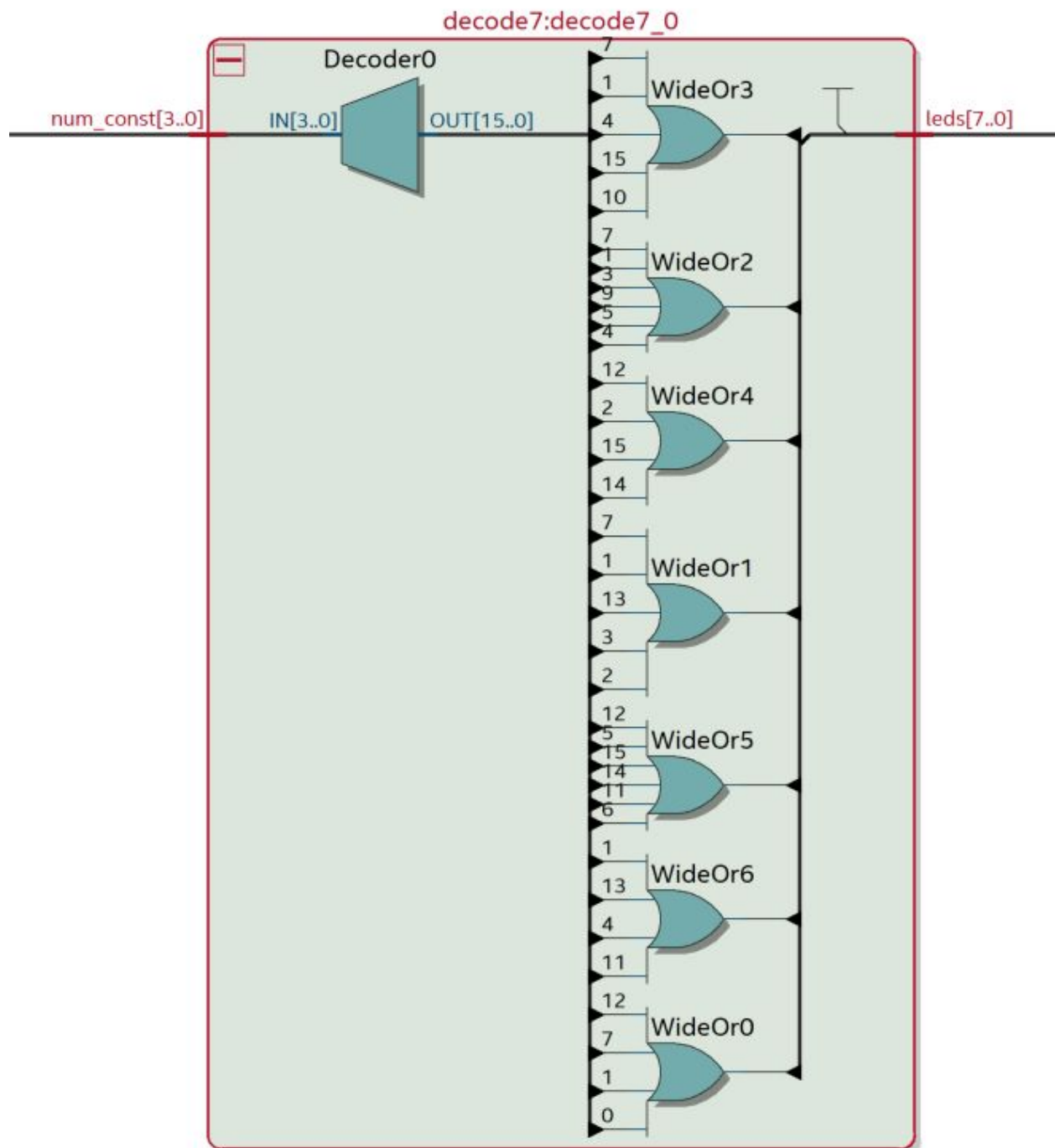


Figure 8: Block diagram for `decode7.sv`



---

## Resources

[HC-SR04 Datasheet](#)

[L298N Motor Driver Datasheet](#)

[Stepper Motor Datasheet](#)

## Conclusion

Our system functioned as expected. The IR sensor prevented the motor from reeling in too far and damaging the chassis. The ultrasonic sensor maintained distance readings with approximately 1 cm of resolution. The 4x4 keypad, switch and 7-segment display all performed within expectation. Finally, the stepper motor was able to accurately raise or lower the line in accordance with changing ground depth. All of these pieces of hardware working together produced a system that maintained a hook at a set distance above the ground, even with changing ground levels, while preventing damage to the system.

---

## Appendix A: Code

The following section which includes all the code used in this project.

### SV Module: Fish.sv Top Level

```
module fish ( output logic [3:0] kpc,    // column select, active-low
              (* altera_attribute = "-name WEAK_PULL_UP_RESISTOR ON" *)
              input logic [3:0] kpr,     // rows, active-low w/ pull-ups
              output logic [7:0] leds,   // active-low LED segments
              output logic [3:0] ct,     // " digit enables
              output logic toggle_in,    // Input to the toggle switch.
              input logic toggle_out,    // Output from the toggle switch.
              input logic reset_n, CLOCK_50,
              output logic proximity_in,
              input logic proximity_out,
              output logic LED1,
              output logic LED2,
              output logic LED3,
              output logic LED4,
              output logic LED5,
              output logic LED6,
              output logic LED7,
              output logic LED8,
              output logic line_a,
              output logic line_b,
              output logic line_c,
              output logic line_d,
              input logic PW,
              output logic trig,
              input logic echo);

    logic clk ;                      // 2kHz clock for keypad scanning
    logic kphit ;                    // a key is pressed
    logic [3:0] num ;                // value of pressed key
    logic [3:0] num_const = 0;      // stored value of the last pressed key
    logic toggle;                    // logic value of the output from the
toggle switch
    logic proximity;                  // logic value of the input from the
proximity sensor
    logic [1:0] dir = 2'b00;         // Motor direction variable
    logic [3:0] signal;               // Motor driver control signal
    logic [39:0] distance;
    logic [31:0] dist_test;
    logic [31:0] leng_test;

    assign ct = { {3{1'b0}}, 1'b1 } ;
    assign toggle_in = 0;
    assign proximity_in = 1;
```

```

pll pll0 ( .inclk0(CLOCK_50), .c0(clk) );
decode7 decode7_0 ( .num_const, .leds);
kpdecode kpdecode_0 ( .kpc, .kpr, .kphit, .num, .num_const, .clk,
.reset_n);
colseq colseq_0 ( .kpr, .clk, .reset_n, .kpc);
mode mode_0 ( .toggle_out, .toggle, .clk, .LED1);
optics optics_0 ( .LED2, .proximity_out, .proximity, .clk);
motor motor_0 ( .clk, .reset_n, .dir, .signal);
motor_decode motor_decode_0 ( .signal, .clk, .line_a, .line_b, .line_c,
.line_d);
control control_0 ( .clk, .toggle, .reset_n, .num, .num_const, .distance,
.dir, .proximity_out, .dist_test, .leng_test);
pulse pulse_0 ( .clk, .trig, .echo, .distance);

```

**endmodule**

```

// megafunction wizard: %ALTPLL%
// ...
// THIS IS A WIZARD-GENERATED FILE. DO NOT EDIT THIS FILE!
// ...

```

**module** pll ( inclk0, c0);

```

    input    inclk0;
    output   c0;

```

```

    wire [0:0] sub_wire2 = 1'h0;
    wire [4:0] sub_wire3;
    wire sub_wire0 = inclk0;
    wire [1:0] sub_wire1 = {sub_wire2, sub_wire0};
    wire [0:0] sub_wire4 = sub_wire3[0:0];
    wire c0 = sub_wire4;

```

```

altpll altpll_component ( .inclk (sub_wire1), .clk
(sub_wire3), .activeclock (), .areset (1'b0), .clkbad
(), .clkena ({6{1'b1}}), .clkloss (), .clkswitch
(1'b0), .configupdate (1'b0), .enable0 (), .enable1 (),
.extclk (), .extclkena ({4{1'b1}}), .fbin (1'b1),
.fbmimichidir (), .fbout (), .fref (), .icdrclk (),
.locked (), .pfdena (1'b1), .phasecounterselect
({4{1'b1}}), .phasedone (), .phasetep (1'b1),
.phaseupdown (1'b1), .pllena (1'b1), .scanaclr (1'b0),
.scanclk (1'b0), .scanclkena (1'b1), .scandata (1'b0),
.scandataout (), .scandone (), .scanread (1'b0),
.scanwrite (1'b0), .sclkout0 (), .sclkout1 (),
.vcooverrange (), .vcounderrange ());

```

**defparam**

```

    altpll_component.bandwidth_type = "AUTO",
    altpll_component.clk0_divide_by = 250,
    altpll_component.clk0_duty_cycle = 50,
    altpll_component.clk0_multiply_by = 1,
    altpll_component.clk0_phase_shift = "0",

```

```

altpll_component.compensate_clock = "CLK0",
altpll_component.inclk0_input_frequency = 20000,
altpll_component.intended_device_family = "Cyclone IV E",
altpll_component.lpm_hint = "CBX_MODULE_PREFIX=lab1clk",
altpll_component.lpm_type = "altpll",
altpll_component.operation_mode = "NORMAL",
altpll_component.pll_type = "AUTO",
altpll_component.port_activeclock = "PORT_UNUSED",
altpll_component.port_areset = "PORT_UNUSED",
altpll_component.port_clkbad0 = "PORT_UNUSED",
altpll_component.port_clkbad1 = "PORT_UNUSED",
altpll_component.port_clkloss = "PORT_UNUSED",
altpll_component.port_clkswitch = "PORT_UNUSED",
altpll_component.port_configupdate = "PORT_UNUSED",
altpll_component.port_fbin = "PORT_UNUSED",
altpll_component.port_inclk0 = "PORT_USED",
altpll_component.port_inclk1 = "PORT_UNUSED",
altpll_component.port_locked = "PORT_UNUSED",
altpll_component.port_pfdena = "PORT_UNUSED",
altpll_component.port_phasecounterselect = "PORT_UNUSED",
altpll_component.port_phasedone = "PORT_UNUSED",
altpll_component.port_phasestep = "PORT_UNUSED",
altpll_component.port_phaseupdown = "PORT_UNUSED",
altpll_component.port_pllena = "PORT_UNUSED",
altpll_component.port_scanaclr = "PORT_UNUSED",
altpll_component.port_scanclk = "PORT_UNUSED",
altpll_component.port_scanclkena = "PORT_UNUSED",
altpll_component.port_scandata = "PORT_UNUSED",
altpll_component.port_scandataout = "PORT_UNUSED",
altpll_component.port_scandone = "PORT_UNUSED",
altpll_component.port_scanread = "PORT_UNUSED",
altpll_component.port_scanwrite = "PORT_UNUSED",
altpll_component.port_clk0 = "PORT_USED",
altpll_component.port_clk1 = "PORT_UNUSED",
altpll_component.port_clk2 = "PORT_UNUSED",
altpll_component.port_clk3 = "PORT_UNUSED",
altpll_component.port_clk4 = "PORT_UNUSED",
altpll_component.port_clk5 = "PORT_UNUSED",
altpll_component.port_clkena0 = "PORT_UNUSED",
altpll_component.port_clkena1 = "PORT_UNUSED",
altpll_component.port_clkena2 = "PORT_UNUSED",
altpll_component.port_clkena3 = "PORT_UNUSED",
altpll_component.port_clkena4 = "PORT_UNUSED",
altpll_component.port_clkena5 = "PORT_UNUSED",
altpll_component.port_extclk0 = "PORT_UNUSED",
altpll_component.port_extclk1 = "PORT_UNUSED",
altpll_component.port_extclk2 = "PORT_UNUSED",
altpll_component.port_extclk3 = "PORT_UNUSED",
altpll_component.width_clock = 5;

```

endmodule

## SV Module: Control.sv

---

```

module control (input logic clk,
                input logic toggle,
                input logic proximity_out,
                input logic reset_n,
                input logic [3:0] num,
                input logic [3:0] num_const,
                input logic [39:0] distance,
                output logic [1:0] dir,
                output logic [31:0] dist_test,
                output logic [31:0] leng_test);

    logic reset = 1; // Required to reel the wire all
the way in on reset
    logic [31:0] max_length = 50; // Max length of the wire
    logic [1:0] dir_next; // Next motor direction
    logic [31:0] test = 0; // Test clock
    logic [31:0] length; // Length of the wire currently out
    logic [31:0] length_next = 0;

always_comb begin

    dir_next = dir;
    length_next = length;

    dist_test = distance/10000000;
    leng_test = length/10000000;

    // Manual mode
    if (toggle) begin

        unique case(num)
            10: dir_next = 2'b10;
            11: dir_next = 2'b11;
            default: dir_next = 2'b00;
        endcase

    end

    // Automatic mode
    if (!toggle) begin

        if ((length/10000000) < (distance/10000000))
            dir_next = 2'b11;

        if ((length/10000000) > (distance/10000000))
            dir_next = 2'b10;

        if ((length/10000000) == (distance/10000000))
            dir_next = 2'b00;

    end

end

```

---

```

// Length Adjustments
unique case(dir)
    2'b00: length_next = length_next;
    2'b10: length_next = length_next - 500;
    2'b11: length_next = length_next + 500;
endcase

if (!proximity_out)
    length_next = 0;

if (length_next[31])
    length_next = 0;

end

always_ff @(posedge clk) begin

    if (!proximity_out && dir_next == 2'b10)
        dir <= 2'b00;
    else if ((length/10000000 > max_length) && (dir_next == 2'b11))
        dir <= 2'b00;
    else
        dir <= dir_next;

    length <= length_next;

end

endmodule

```

## SV Module: Colseq.sv

```

module colseq    (input logic [3:0] kpr,
                  input logic  clk,
                  input logic  reset_n,
                  output logic [3:0] kpc);

    logic [3:0] kpc_next;

    always_comb begin

        // Check for a reset press
        if(!reset_n)
            kpc_next = 4'b0111;

        // Hold the current column if any rows are low
        else if (kpr != 4'b1111)
            kpc_next = kpc;

        // Change the low column to the next in sequence
        else

```

```

        case(kpc)
            4'b0111: kpc_next = 4'b1011;
            4'b1011: kpc_next = 4'b1101;
            4'b1101: kpc_next = 4'b1110;
            4'b1110: kpc_next = 4'b0111;
            default: kpc_next = 4'b0111;
        endcase
    end

    always @(posedge clk) begin
        kpc <= kpc_next;
    end

endmodule

```

## SV Module: Decode7.sv

```

module decode7 (input logic [3:0] num_const,
               output logic [7:0] leds);

    always_comb begin
        unique case (num_const) // Segments are active low
            0: leds = 8'b1100_0000; // Segments for a 0
            1: leds = 8'b1111_1001; // Segments for a 1
            2: leds = 8'b1010_0100; // Segments for a 2
            3: leds = 8'b1011_0000; // Segments for a 3
            4: leds = 8'b1001_1001; // Segments for a 4
            5: leds = 8'b1001_0010; // Segments for a 5
            6: leds = 8'b1000_0010; // Segments for a 6
            7: leds = 8'b1111_1000; // Segments for a 7
            8: leds = 8'b1000_0000; // Segments for a 8
            9: leds = 8'b1001_0000; // Segments for a 9
            10: leds = 8'b1000_1000; // Segments for a A
            11: leds = 8'b1000_0011; // Segments for a B
            12: leds = 8'b1100_0110; // Segments for a C
            13: leds = 8'b1010_0001; // Segments for a D
            14: leds = 8'b1000_0110; // Segments for an E
            15: leds = 8'b1000_1110; // Segments for a F
            default: leds = 8'b1100_0000; // Default is 0
        endcase
    end

endmodule

```

## SV Module: kpdecode.sv

```

module kpdecode (input logic [3:0] kpc,
                input logic [3:0] kpr,
                input logic clk, reset_n,
                output logic kphit,
                output logic [3:0] num,
                output logic [3:0] num_const);

    always_comb begin
        // Selects the correct LED output
    end

```

---

```

// for a given row and column input
unique case (kpr) // Active low
    4'b1110:    unique case (kpc) // Active low
                4'b1110: num = 13;
                4'b1101: num = 15;
                4'b1011: num = 0;
                4'b0111: num = 14;
                default: num = 99;
            endcase

    4'b1101:    unique case (kpc) // Active low
                4'b1110: num = 12;
                4'b1101: num = 9;
                4'b1011: num = 8;
                4'b0111: num = 7;
                default: num = 99;
            endcase

    4'b1011:    unique case (kpc) // Active low
                4'b1110: num = 11;
                4'b1101: num = 6;
                4'b1011: num = 5;
                4'b0111: num = 4;
                default: num = 99;
            endcase

    4'b0111:    unique case (kpc) // Active low
                4'b1110: num = 10;
                4'b1101: num = 3;
                4'b1011: num = 2;
                4'b0111: num = 1;
                default: num = 99;
            endcase

    default:    num = 99;
endcase

// Modifies kbhit based on if a key is
// being pressed or not
if (kpr == 4'b1111)
    kphit = 0;
else
    kphit = 1;

end

always_ff @(posedge clk) begin
    if (kphit)
        num_const <= num;
    else if (!reset_n)
        num_const <= 0;
    else
        num_const <= num_const;
end

```



---

```
endmodule
```

### SV Module: mode.sv

```
module mode (input logic toggle_out,
             input logic clk,
             output logic LED1,
             output logic toggle);

    always_ff @(posedge clk) begin

        toggle <= toggle_out;
        LED1 <= toggle;

    end

endmodule
```

### SV Module: motor.sv

```
module motor(input logic clk,
             input logic reset_n,
             input logic [1:0] dir,
             output logic [3:0] signal);

    localparam pos_stop = 0;
    localparam pos_1 = 1;
    localparam pos_2 = 2;
    localparam pos_3 = 4;
    localparam pos_4 = 8;

    logic[3:0] pos_next;
    logic [8:0] count;

    always_comb begin

        if(!reset_n) begin

            pos_next = pos_stop;

        end

        else begin

            if (dir[1]) begin

                if (dir [0]) begin
                    unique case (signal)
                        pos_stop: pos_next = pos_1;
                        pos_1: pos_next = pos_2;
                        pos_2: pos_next = pos_3;
                        pos_3: pos_next = pos_4;
                        pos_4: pos_next = pos_1;
                    endcase
                end
            end
        end
    end
endmodule
```

---

```

        default: pos_next = '0;
    endcase
end

else begin

    unique case (signal)
        pos_stop: pos_next = pos_4;
        pos_1: pos_next = pos_4;
        pos_2: pos_next = pos_1;
        pos_3: pos_next = pos_2;
        pos_4: pos_next = pos_3;
        default: pos_next = '0;
    endcase

end

end

else begin

    pos_next = pos_stop;

end

end

end

always_ff @(posedge clk) begin

    if (count == 511)
        signal <= pos_next;
    else
        signal <= signal;

    count <= count + 1;

end

endmodule

```

## SV Module: motor\_decode.sv

```

module motor_decode(input logic [3:0] signal,
                    input logic clk,
                    output logic line_a,
                    output logic line_b,
                    output logic line_c,
                    output logic line_d);

    always_ff @(posedge clk) begin
        line_a <= signal[0];
    end
endmodule

```

---

```
    line_b <= signal[2];
    line_c <= signal[1];
    line_d <= signal[3];
end
```

```
endmodule
```

## SV Module: optics.sv

```
module optics    (input logic proximity_out,
                  input logic clk,
                  output logic proximity,
                  output logic LED2);
```

```
    always_ff @(posedge clk) begin
```

```
        proximity <= proximity_out;
        LED2 <= proximity;
```

```
    end
```

```
endmodule
```

## SV Module: pulse.sv

```
module pulse (input logic clk,
              output logic trig,
              input logic echo,
              output logic [39:0] distance);
```

```
    logic [13:0] count= '0;
    logic [31:0] pulsewidth = '0;
```

```
    always_ff @(posedge clk) begin
```

```
        if (count == 0 || count == 1)
            trig <= '1;
```

```
        else
            trig <= '0;
```

```
        count <= count + 1;
```

```
        if (echo)
            pulsewidth <= pulsewidth + 1;
```

```
        else if (~echo)
            pulsewidth <= 0;
```

```
    end
```

```
    always_ff @(negedge echo) begin
        distance <= pulsewidth * 5 / 58 * 10000000;
    end
```

---

endmodule